



EE 240A

Final Project Presentation

Chandrasahas Vadali
12/13/2024

Contents

- Op-amp Overview
- Design Methodology
- Results and Discussion
- Potential Improvements
- Acknowledgements

Op-amp Overview

- 2-stage op-amp with Miller Compensation
- Input stage: Telescopic Cascode for high gain
- Output stage: Class-AB common source for improved slew rate

AC Results Summary

Parameter	Value
DC Gain	86 dB
GBW	18.54 MHz
CMRR	70 dB
PSRR	51 dB (VDDL) 64 dB (VDDH)
Phase Margin	52.3 deg

Transient Results Summary – 350 mV input


Parameter	Value
Settling time	159.2 ns
Avg Power Consumed	0.312 mW
Current Efficiency (Imax/Ibias)	10.66
SR+ Max	17.6 V/us
SR- Max*	17.2 V/us
FoM	20.08

Misc. Results

Parameter	Value
Area	970 um^2
Mismatch	Poor

*estimate

Op-amp Overview - Schematic


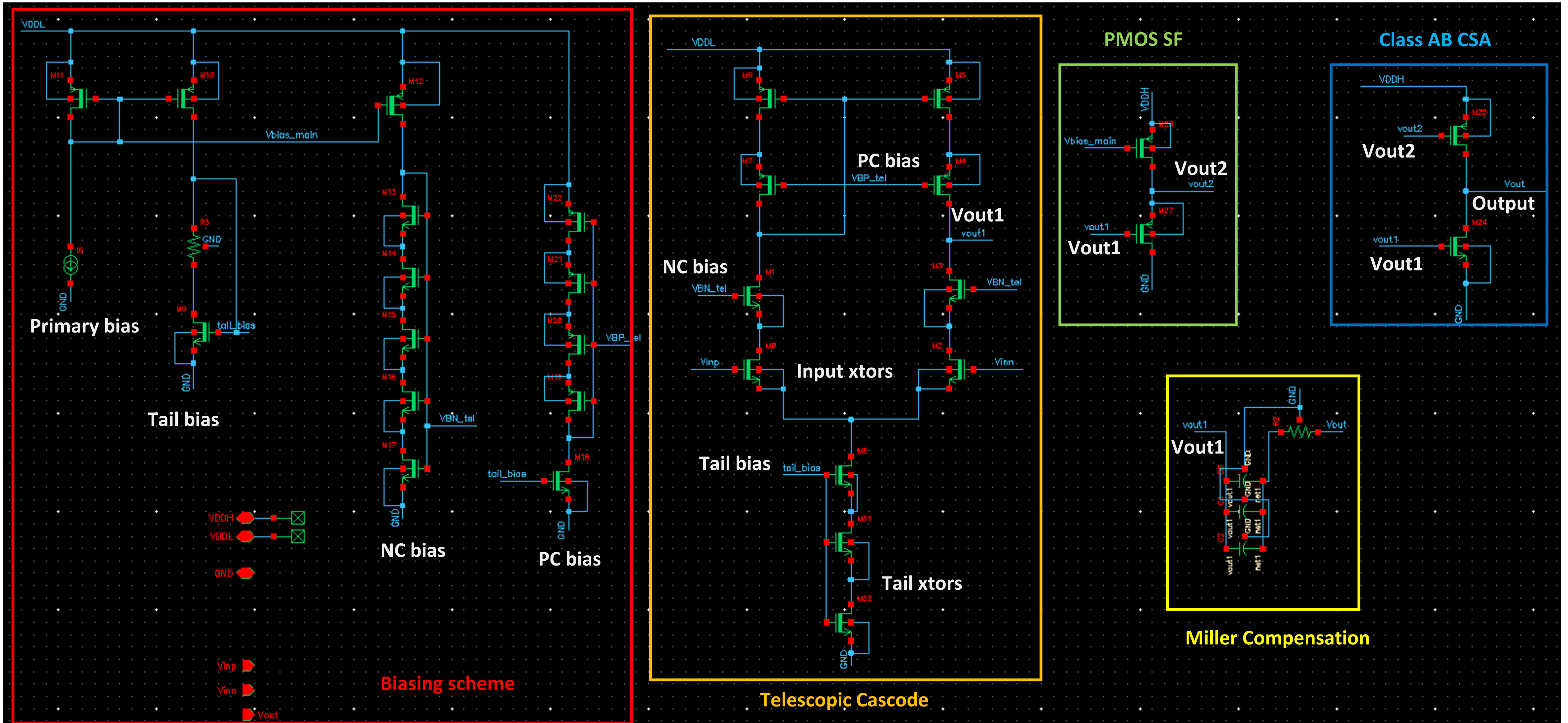


High-level Specs

Spec	Value
Settling Time	< 180 ns
Total Error	< 0.2%


$$f_u \approx \frac{-\ln(\epsilon_d)}{T_{set}} = \frac{-\ln(0.002 - \epsilon_s)}{T_{set}}$$
$$A_0 = \frac{1}{f} \left(\frac{1 - \epsilon_s}{\epsilon_s} \right)$$
$$\frac{dV_{out}}{dt} = \frac{1.4 V}{T_{set}} = 7.76 V/\mu S$$

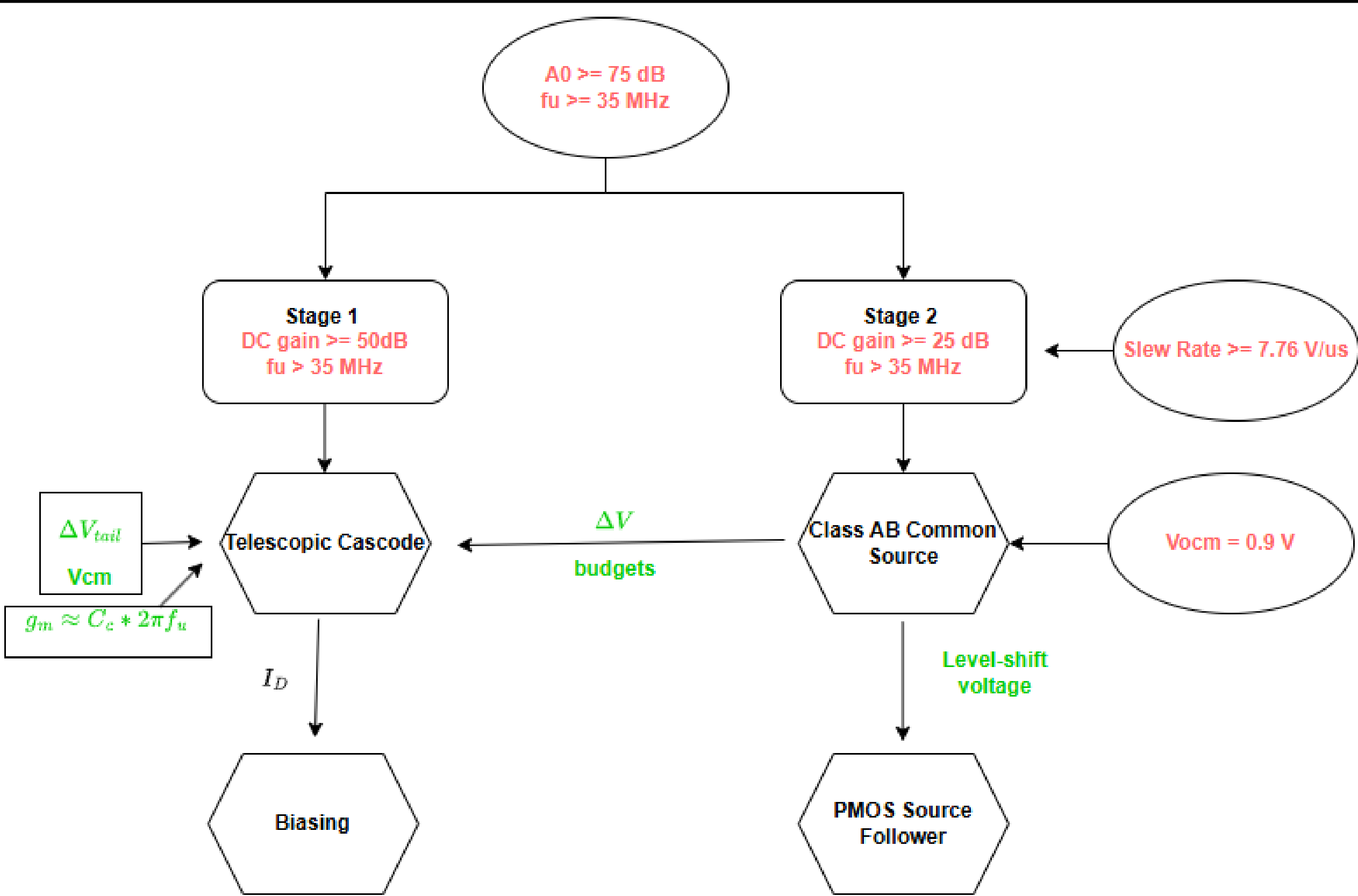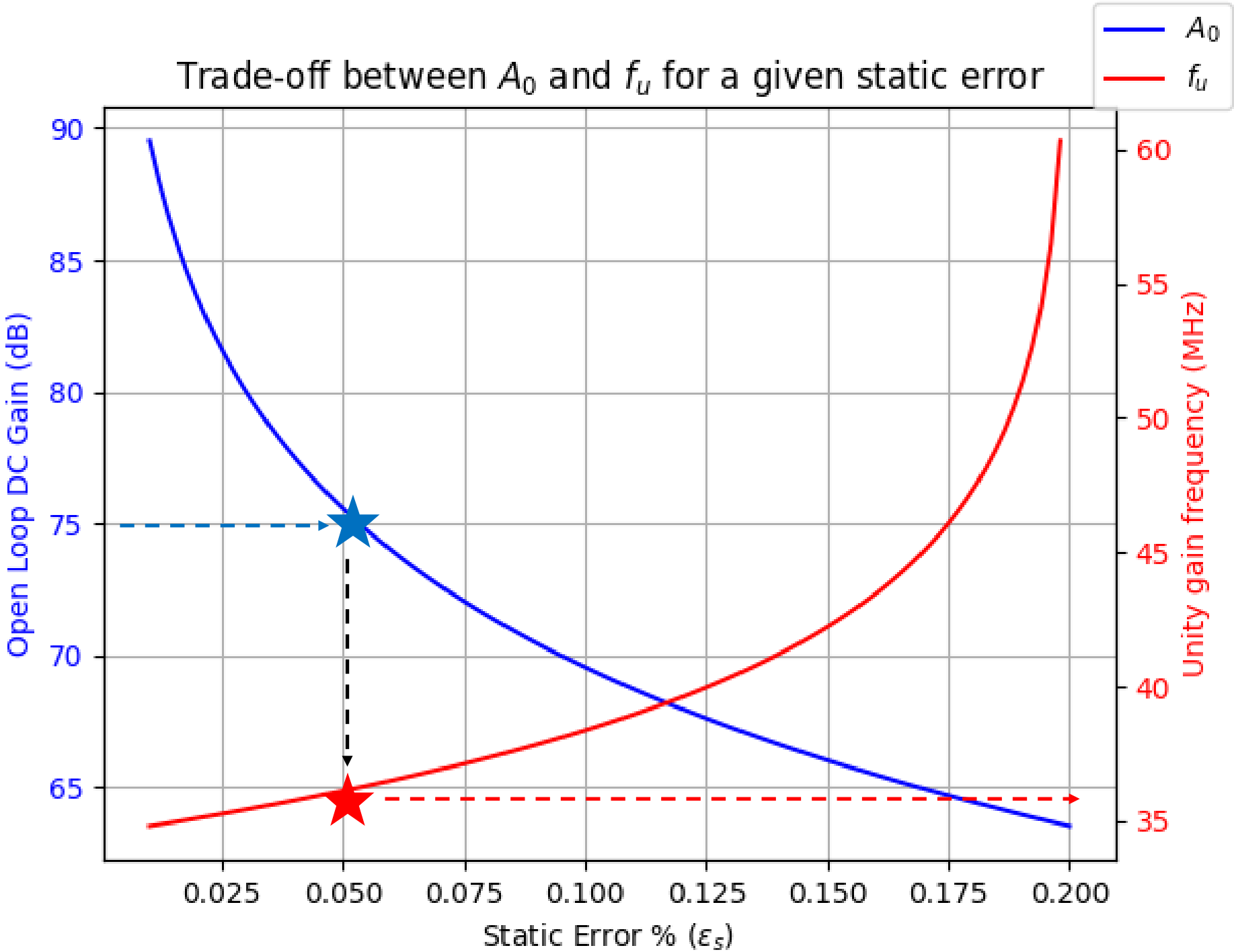ϵ_s - static error
 ϵ_d - dynamic error
 A_0 - open loop DC gain
 f - feedback factor
 V_{out} - output voltage
 T_{set} - settling time




- More constraints → narrower design space
- gm/ID methodology to size xtors and bias voltages
- Start design with output stage → has max constraints
- Biasing voltages of output stage give more constraints for input stage
- Compensation design → set by phase margin, sets gm of input stage
- Make Design choices in stage 1- power supply, tail VDS drop, etc.

Class AB CSA- Design

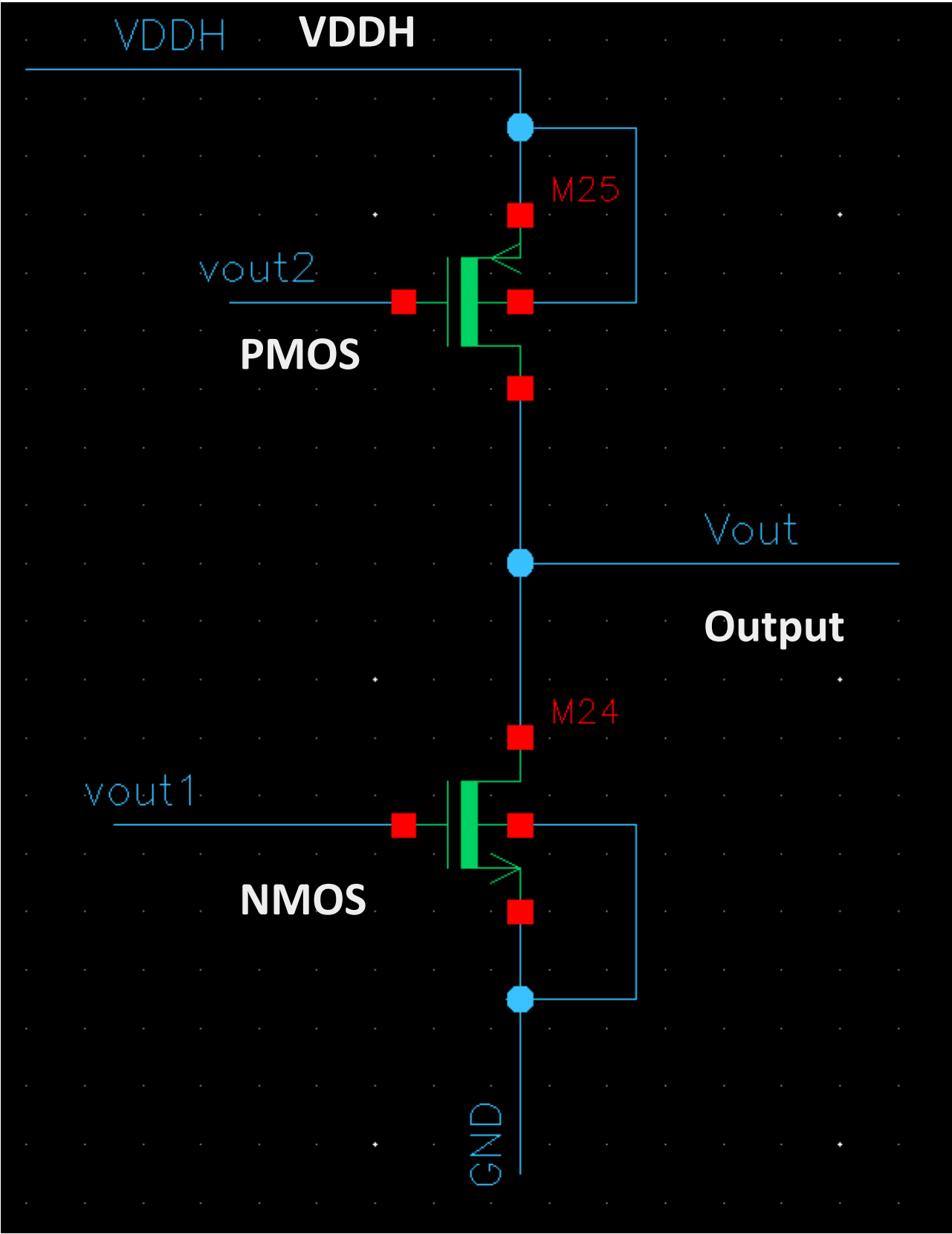


Parameter	Value
Ln, Lp	0.7 um
Wn	28 um
Wp	24 um
VGS,n	0.597 V
VGS,p	0.512 V

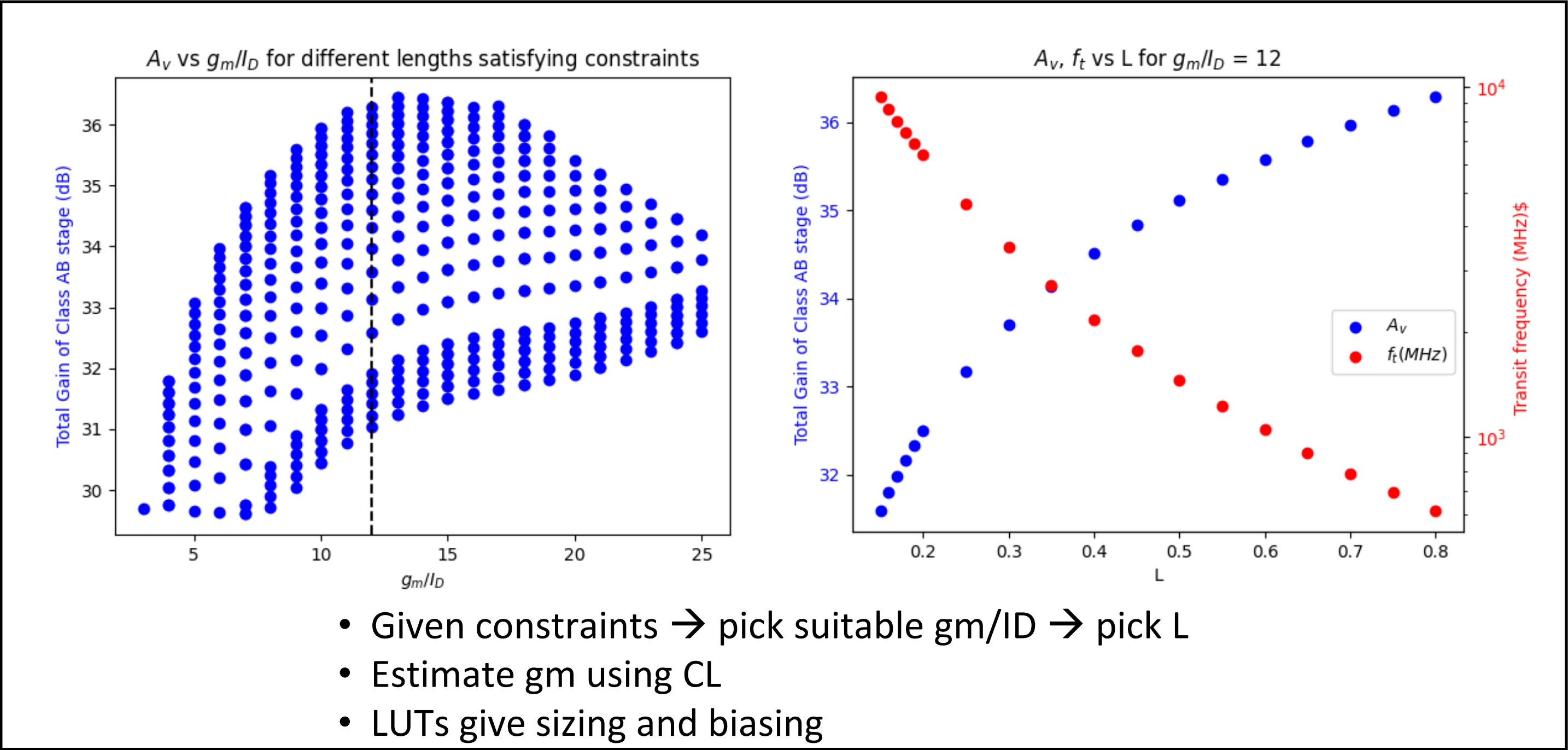


Source Follower – Level-shifting


Which biasing scheme to pick?

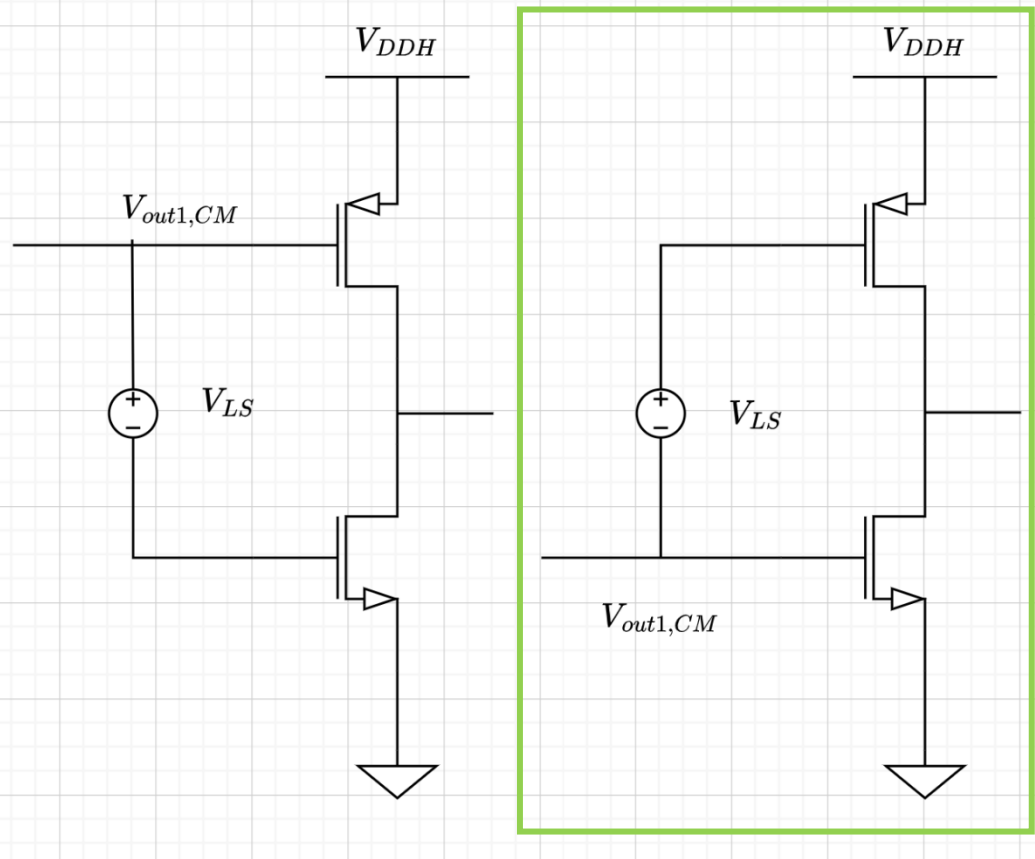

 - **Vout1,CM to PMOS (left)**
 \rightarrow needs higher Vout1,CM
 \rightarrow can't use VDDL for first stage
- **Vout1,CM to NMOS (right)**
 \rightarrow low Vout1,CM low \rightarrow VDDL for first stage \rightarrow save power!




Telescopic Cascode - Design

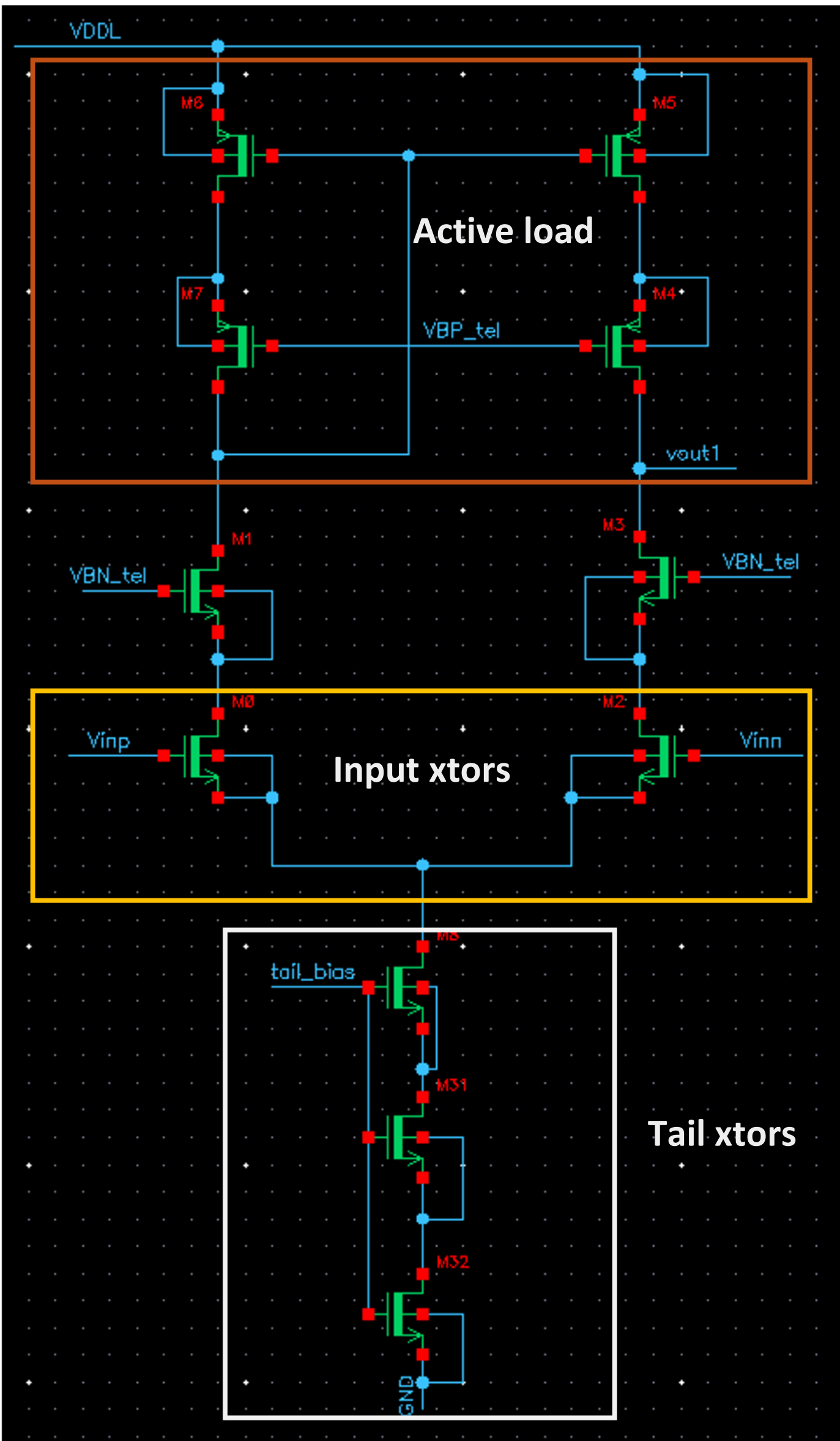

- Designed for high $g_m/I_D \rightarrow$ max gain, min power
- ΔV across tail = 100 mV
- Estimate g_m using C_c (500 fF starting value)
- LUTs give sizing and biasing
- Operates in sub-threshold region for max g_m/I_D [1]


Parameter	Value
L_n, L_p	2 μm
W_n (input)	36 μm
W_p (load)	6.7 μm
g_m/I_D (input)	≈ 22
I_{bias} (tail current/2)	5 μA
V_{icm}	0.5 V

Active Load Design

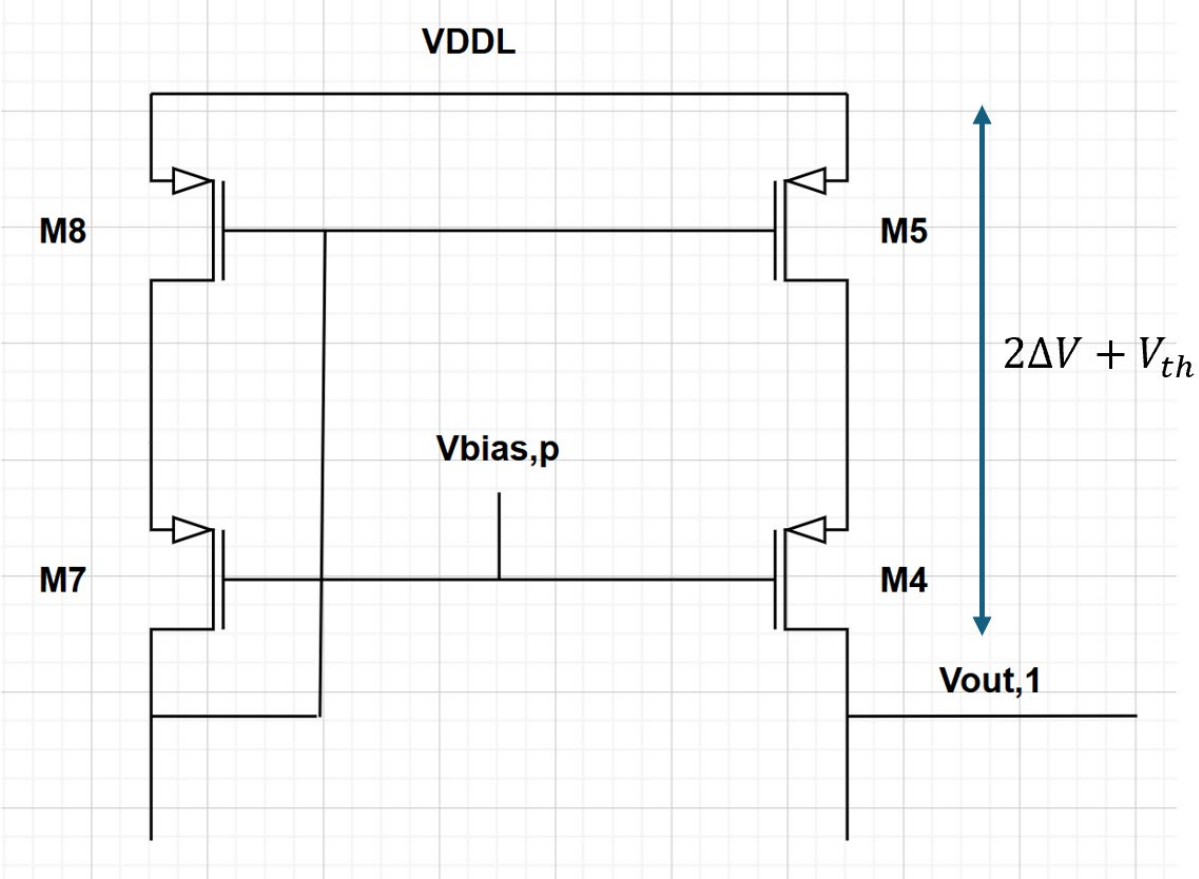

- Save a V_{th} (≈ 430 mV) drop across the load!


Tail xtor – Poor man’s cascode

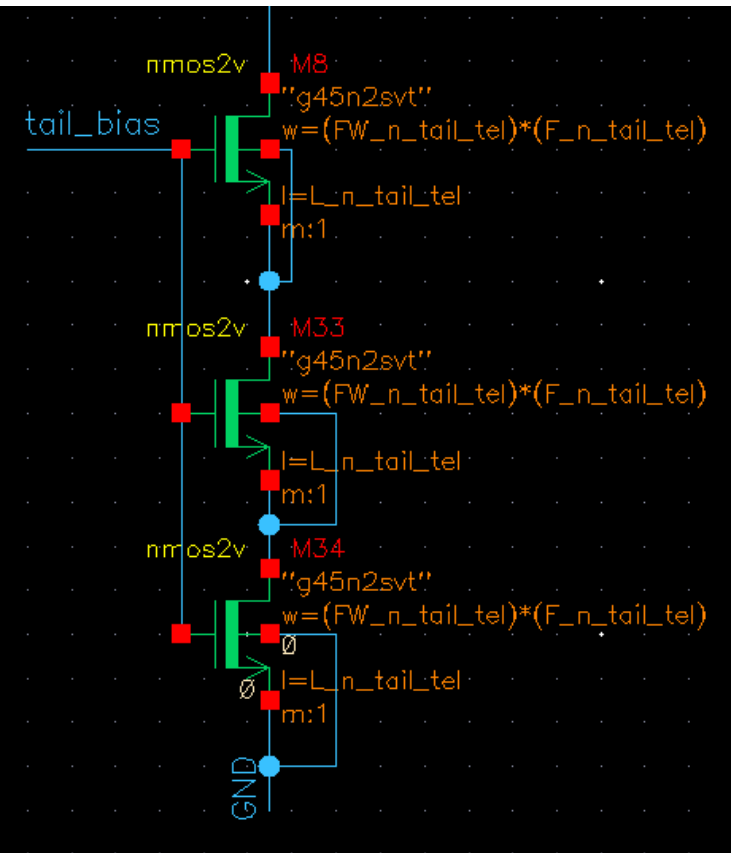

- Increase V_{DS} drop across to 100 mV
- Improve CMRR

[1] F. Silveira, D. Flandre, and P.G.A. Jespers. A $g_{sub}m/i_{sub}d$ based methodology for the design of cmos analog circuits and its application to the synthesis of a silicon-on-insulator micropower ota. IEEE Journal of Solid-State Circuits, 31(9):1314–1319, 1996.


Biasing network

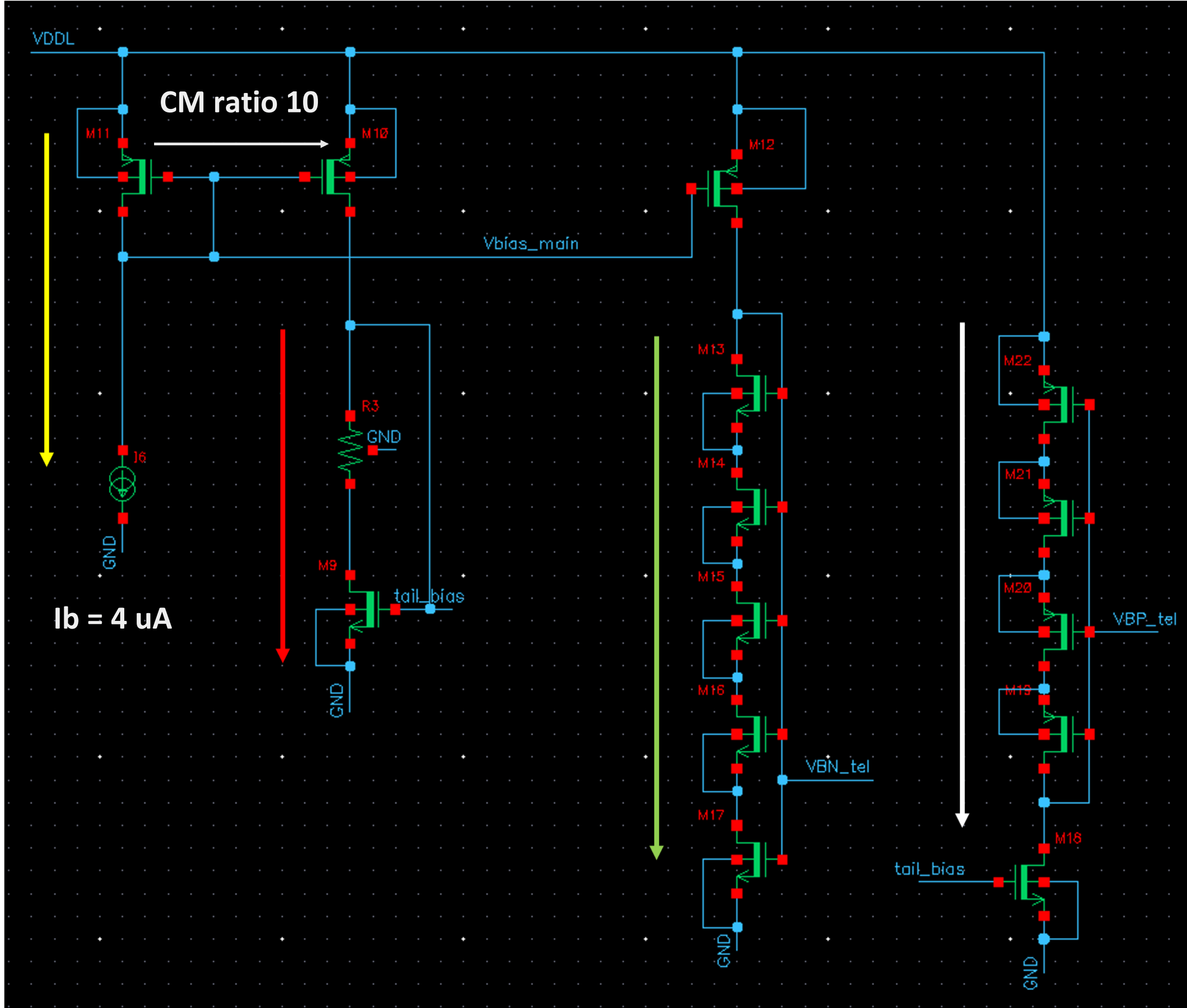


Branch	Purpose
Yellow	Primary bias generator
Red	Bias tail xtors in first stage
Green	Bias NMOS cascode devices in first stage
White	Bias PMOS cascode devices in first stage

Design choices

 1. Current mirror ratio = 10 from primary bias generator to other branches




 2. Resistor to better match VDS across current mirror for tail xtor



3. Cascode NMOS device needs $2\Delta V + \Delta V_{tail}$



Miller Compensation

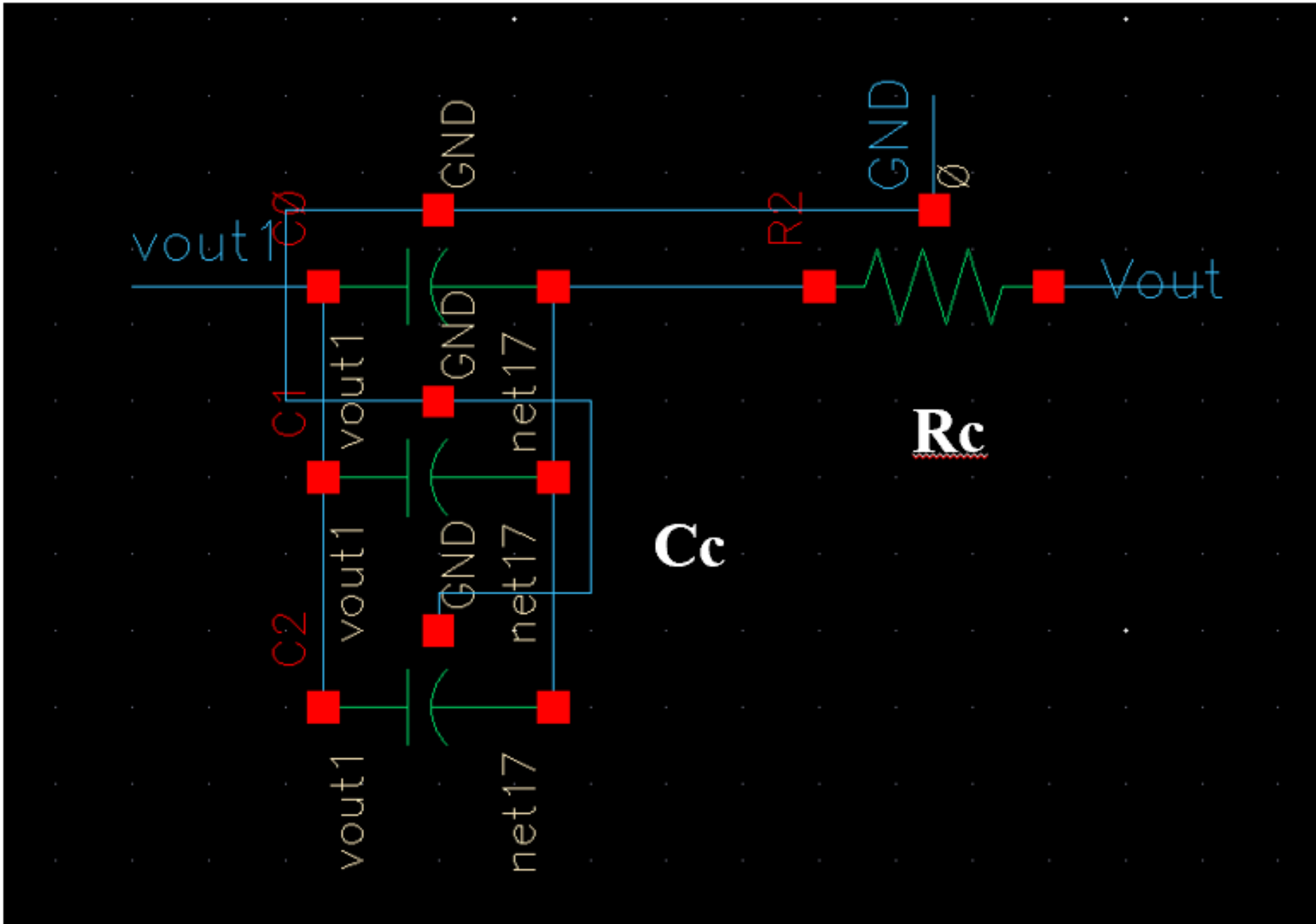

- Start with Cc 500 fF
- $R_c = 1/gm_{out}$ to push the RHP from compensation to infinity
- Tune these values as necessary looking at frequency response

Parameter	Value
Cc	75 fF
Rc	500 ohm

Frequency response

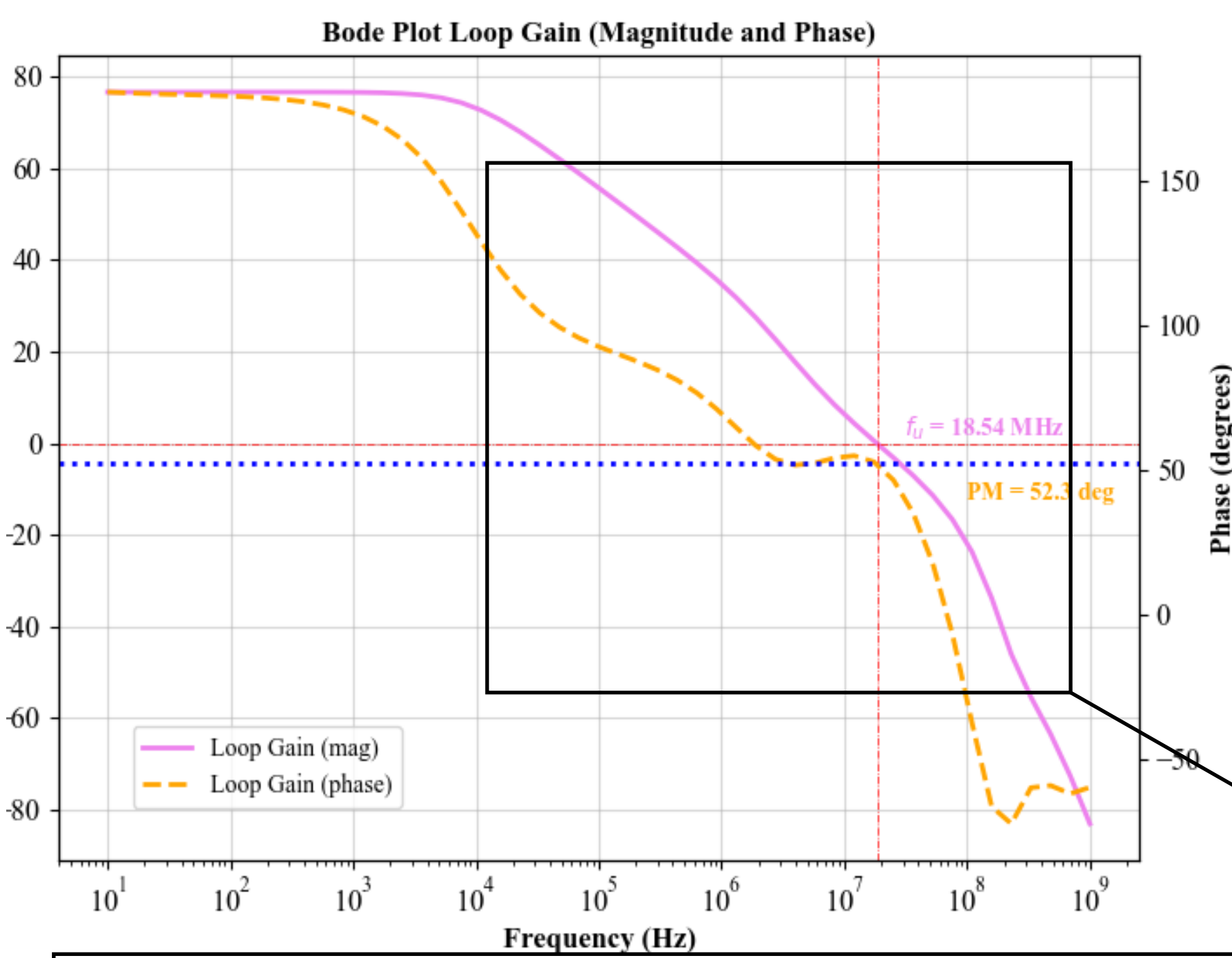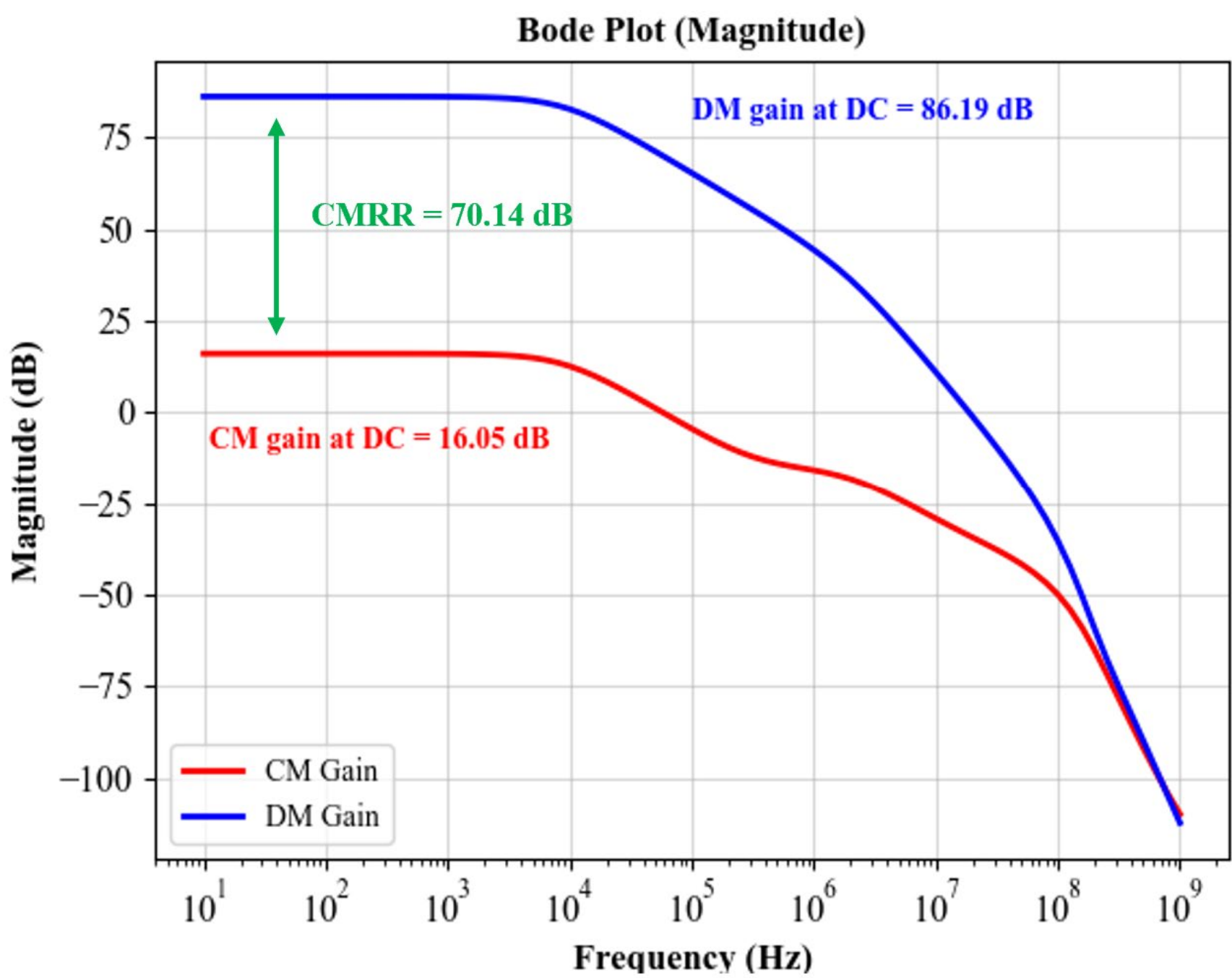

Parameter	Value
DC Gain	86 dB
f_u	18.54 MHz
CMRR	70 dB
Phase Margin	52.3 deg
Dom pole	9.03 kHz
Non-dom pole	1.84 MHz
Dom zero	19.2 MHz

Miller Cap sets first pole


$$f_{p1} \approx \frac{f_u}{A_0\beta} = \frac{g_{m1}}{2\pi A_0\beta \times (C_c + C_{gs,SF})} = \frac{3 * 111.59 \mu S}{2\pi * 20390 * (75 + 20) fF} = 27.50 \text{ kHz}$$

- If we include other parasitics, we can get a better estimate of dominant pole, unity gain freq.
- However, since C_c is smaller than parasitic caps at the output stage, second pole is before unity gain frequency!



Capacitor	Value
C_c	75 fF
$C_{gs,SF}$	20 fF
$C_{GS,AB}$ (NMOS + PMOS)	288 fF

LHP zero helps phase margin!

 
- Proven by phase bump and magnitude plot!
- Where is it coming from?
Zero from Miller compensation and its cancellation are at a very high frequency (GHz)
Maybe PMOS active load? (g_m/C_{gs} around 4 MHz)
- How does it affect transient response?



Transient Response

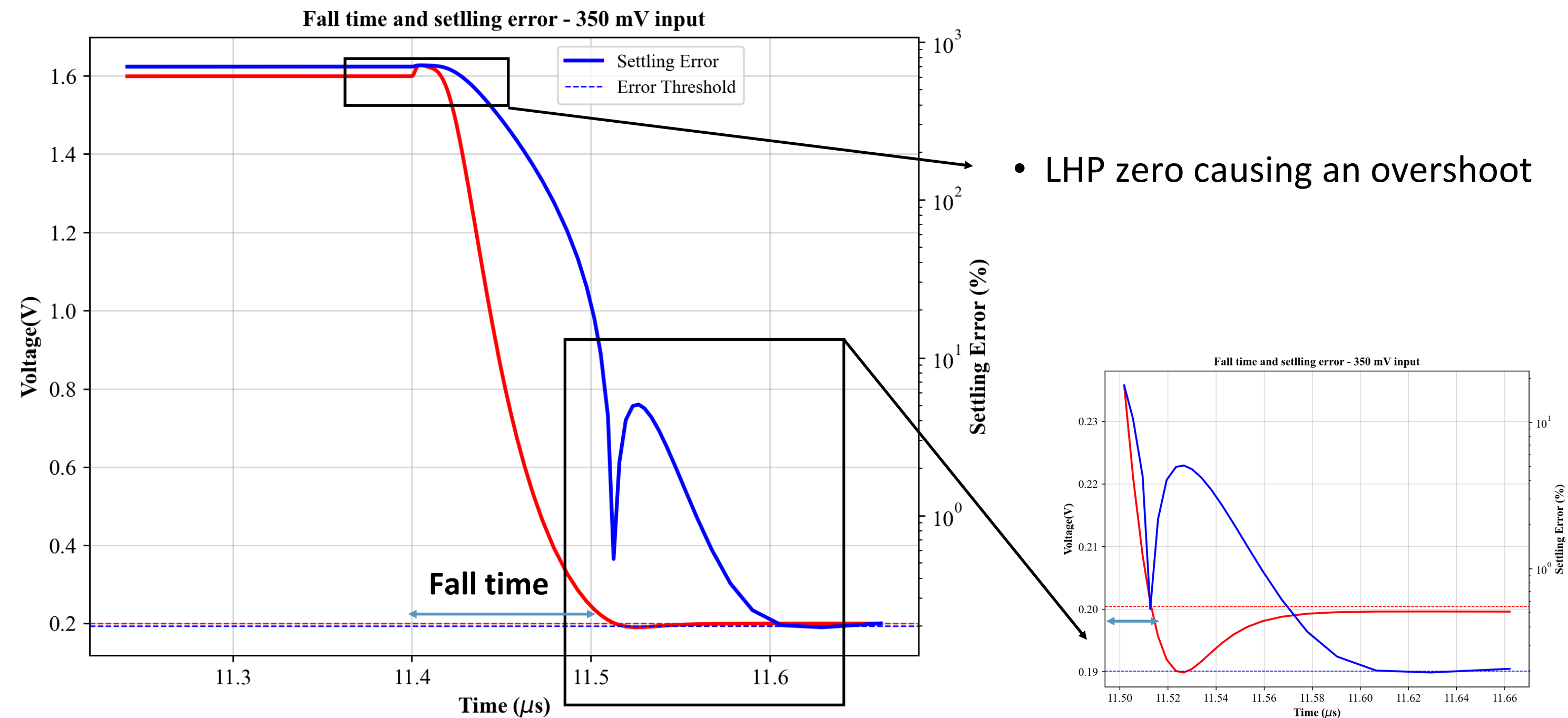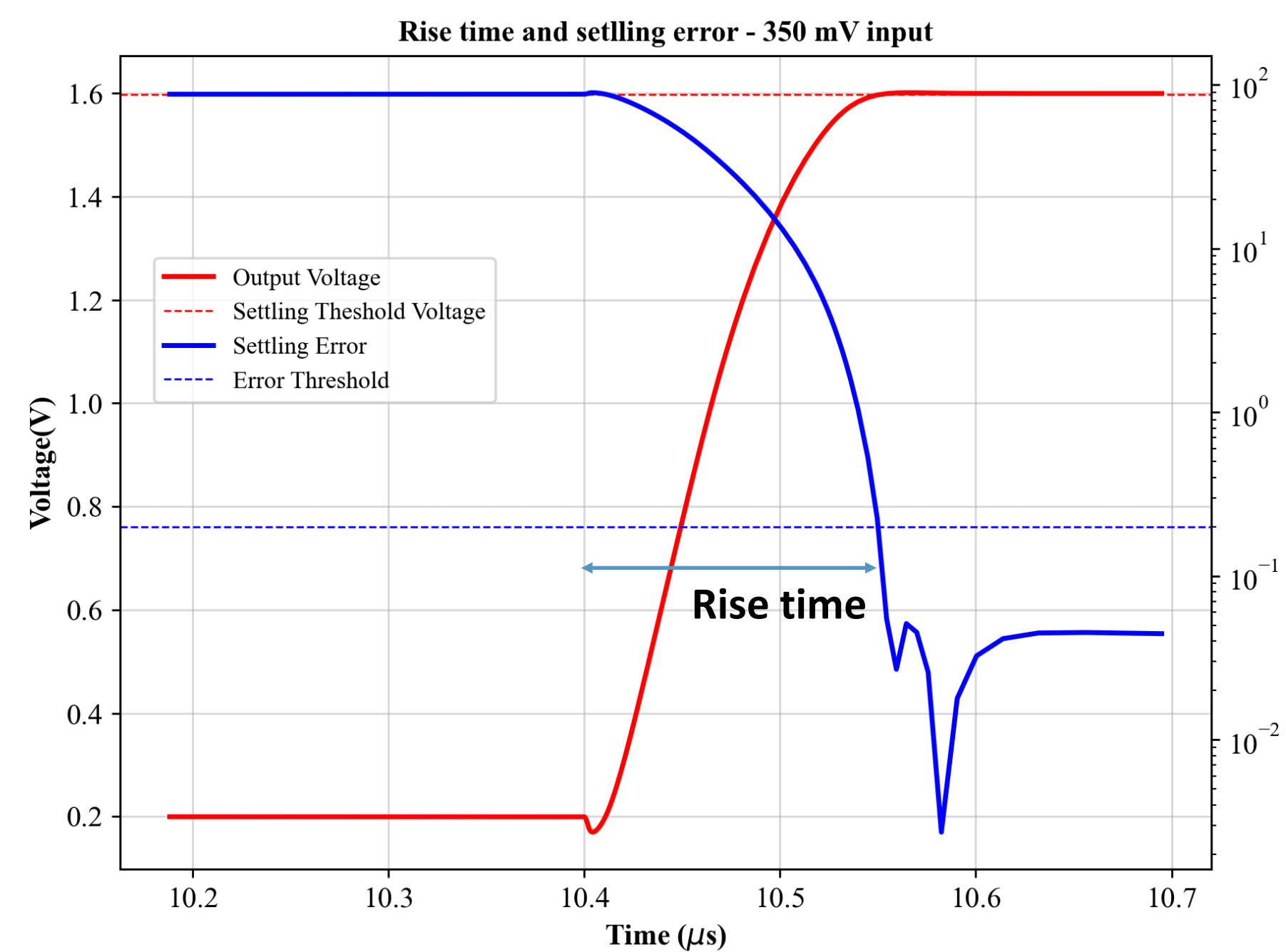


Parameter	5 mV input step	350 mV input step
Rise Time	104.6 ns	152.5 ns
Fall Time	102.9 ns	159.2 ns
Settling Time	104.6 ns	159.2 ns
SR+ max	-	17.6 V/us
SR- max	-	17.2 V/us
CE (Imax/Ibias)	-	10.66
Error	< 0.1%	< 0.1%
Avg Power (VDDL)	0.110 mW	0.110 mW
Avg Power (VDDH)	0.154 mW	0.202 mW
Avg Total Power	0.264 mW	0.312 mW
FoM	36.10	20.08

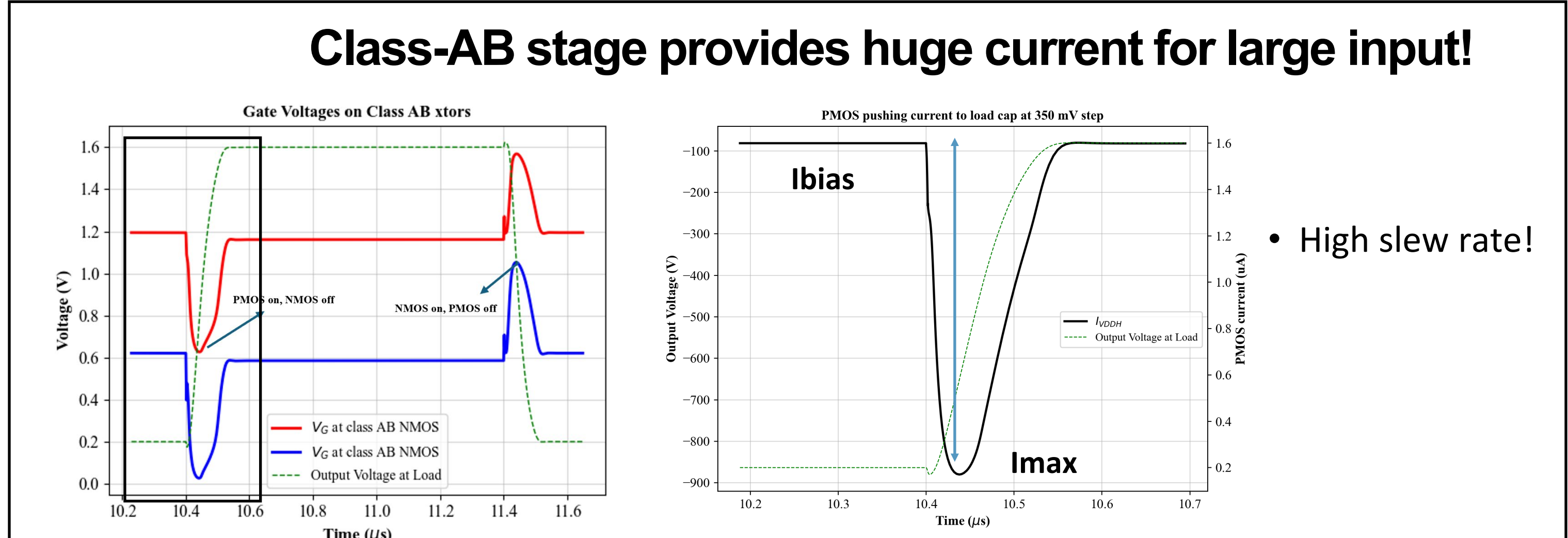

Potential Improvements

Improving class AB slew rate [3]

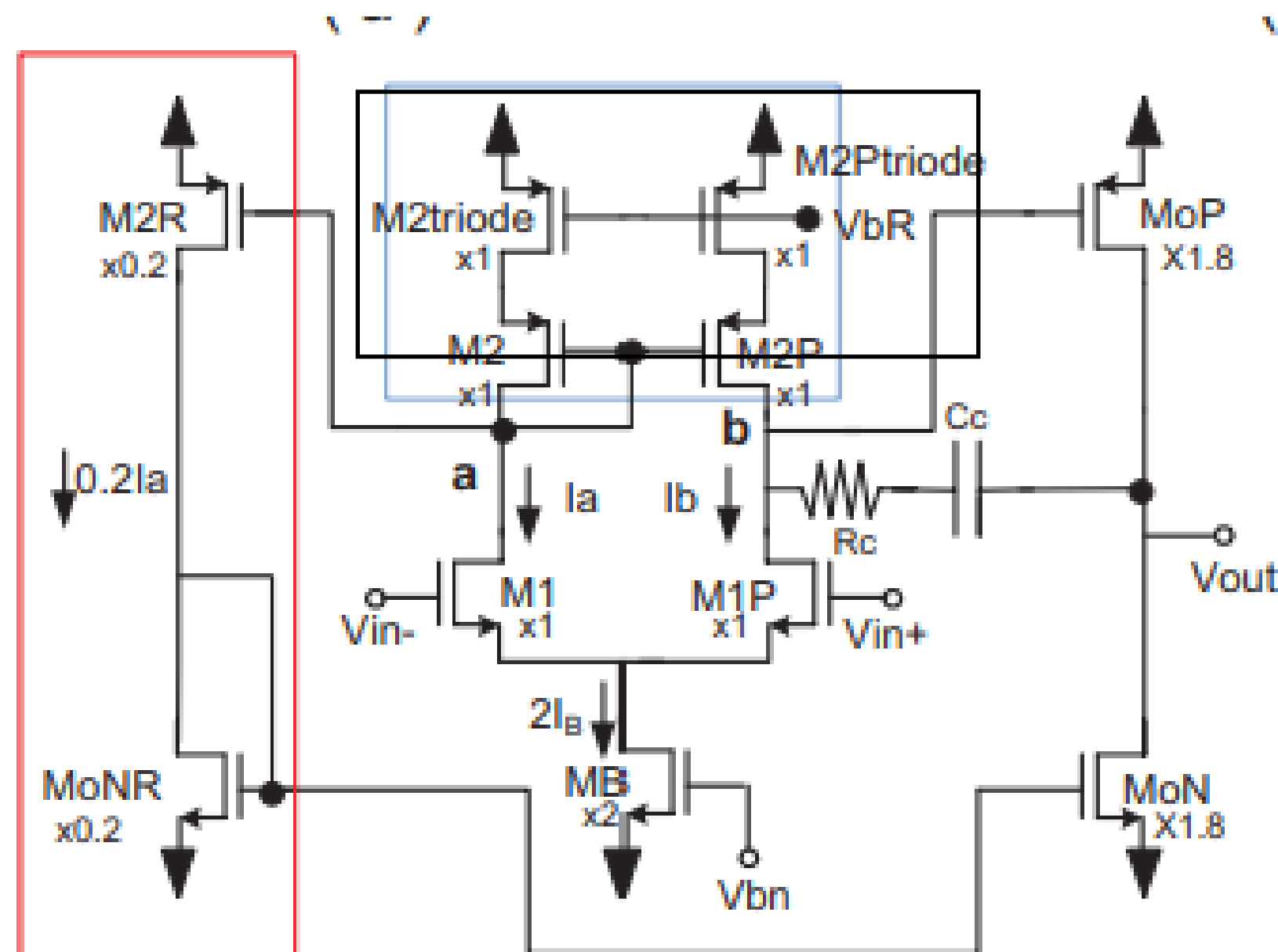


- M2/M2P – biased on brink of saturation
- If they're thrown into triode (say current in branch changes), to support the tail current, their VDS drop has to increase!
- This sets a large VGS for MoP and is copied by the red branch to MoN

Better control over frequency response

- During initial sizing of xtors, width was not extracted by iteratively accounting for parasitic Cgs → underestimated parasitics and therefore, Cc
- Rc could have been tuned to control LHP zero!

$$R_c = \frac{1}{gm_{out}} \left(1 + \frac{C_L}{C_c}\right)$$

Marginal gains in Power/Area

 

- Self-biased current mirror at telescopic active load [2]
- Can reduce power and area by removing one biasing branch
- Resistor occupies area – total savings about 6% estimated for typical values of Rb
- 6% power improvement estimated

[2] Bhawna Aggarwal, Maneesha Gupta, and A.K. Gupta. A comparative study of various current mirror configurations: Topologies and characteristics. *Microelectronics Journal*, 53:134–155, 2016.

[3] Aguado-Ruiz, J., Lopez-Martin, A., Lopez-Lemus, J., & Ramirez-Angulo, J. (2014). Power efficient class AB op-amps with high and symmetrical slew rate. *IEEE Transactions on Very Large Scale Integration (VLSI) Systems*, 22(4), 943–947. doi:10.1109/tvlsi.2013.2256946

Acknowledgements

- Thanks to Prof. Muller for setting us up for success with her class!
- Chun-yen and Rahul helped with the take-off on this project – thanks a lot to both!
- Joosung, Sarah, Aniket – thanks for enduring the endless discussions on the design!

Back up

3 Transistor and Bias Summary

Table 3 shows a summary of dimensions and operating points for each transistor in the amplifier. Table 4 summarizes the passive components used.

XTOR	Purpose	L (μm)	W (μm)	I_D (μA)	V_{GS} (V)	g_m (μS)	g_m/I_D	g_{DS} (μS)
M0	Vinp	1	36	5.09	0.405	111.53	21.91	7.78
M1	NMOS cascode	1	36	5.09	0.393	111.89	21.98	3.61
M2	Vinn	1	36	5.09	0.405	111.52	21.91	7.78
M3	NMOS cascode	1	36	5.09	0.393	111.88	21.98	3.62
M8	Cascode tail	1	90	10.18	0.403	218.43	21.46	72.38
M33	Cascode tail	1	90	10.18	0.427	185.59	18.23	325.87
M34	Cascode tail	1	90	10.18	0.444	167.86	16.49	519.64
M4	PMOS cascode	1	6.7	5.09	-0.504	95.77	18.81	3.36
M5	PMOS cascode	1	6.7	5.09	-0.501	97.3	19.12	1.93
M6	PMOS cascode	1	6.7	5.09	-0.501	97.3	19.12	1.94
M7	PMOS cascode	1	6.7	5.09	-0.504	95.73	18.81	3.41
M11	Primary Bias Generator	1	1.34	3.99	-0.578	43.24	10.84	0.8
M10	Current source	1	13.4	33.37	-0.578	358.98	10.76	6.56
M12	Current source	1	13.4	32.24	-0.578	376.59	11.68	7.19
M9	Bias for tail xtor	1	90	33.37	0.444	647.59	19.41	29.53
M13	Bias for NMOS cascode	1	36	32.24	0.485	532.01	16.50	13.66
M14	Bias for NMOS cascode	1	36	32.24	0.534	361.02	11.20	493.90
M15	Bias for NMOS cascode	1	36	32.24	0.567	285.34	8.85	860.40
M16	Bias for NMOS cascode	1	36	32.24	0.592	243.47	7.55	1143.6
M17	Bias for NMOS cascode	1	45	32.24	0.61	214.01	6.64	1784
M22	Bias for PMOS cascode	1	6.7	20.61	-0.807	46.67	2.26	328
M21	Bias for PMOS cascode	1	6.7	20.61	-0.75	60.27	2.92	269
M20	Bias for PMOS cascode	1	6.7	20.61	-0.682	89.18	4.33	182.7
M19	Bias for PMOS cascode	1	6.7	20.61	-0.592	218.11	10.58	4.06
M18	Current source	1	54	20.61	0.444	397.94	19.31	15.9
M26	PMOS load for SF	4	1.8	18.20	-1.278	19.26	1.05	19.58
M27	SF PMOS	1	2.6	18.20	-0.597	121.90	6.69	2.13
M24	Class AB CSA PMOS	0.7	28	46.42	-0.628	740.66	16.08	11.28
M25	Class AB CSA NMOS	0.7	24	131.41	0.596	1411.07	10.73	24.20

Table 3: Transistor Parameters

Component	Purpose	Value	L (μm)	W (μm)
R3	Matching VDS for tail XTORs biasing	6000	30	1
C0	Miller Cap	30	5	5
C1	Miller Cap	30	5	5
C2	Miller Cap	15	2	5.5
R2	Resistor to cancel RHP from Miller Cap	500	2	5

Table 4: Component Parameters

PSRR

